

Admission Test Sample Question

BRAC University

M.Sc/M.Engg in Electrical & Electronics Engineering

Semester:

Year:

Name: _____

ID: _____

Seat No.: _____

<u>Instructions</u> <ul style="list-style-type: none">• Total duration for the exam is 1 hour• There are two sections in the question• Students have to pass each section separately• Answer each question within the space provided in this question booklet• No additional page will be provided	Marks Distribution		Marks Obtain
	Section 1	30	
	Section 2	30	
	Total	60	

- Adoption of any unfair means in the examination hall will make the candidate disqualified for admission.
- Please do not turn over the page until you are asked to do so.

Good Luck

Section 1

PART A (Total number of questions in this part is **TWO (2)**; answer any **ONE (1)** question)

1. Use Node analysis to find the current I_o as shown in Fig. 1.

[15]

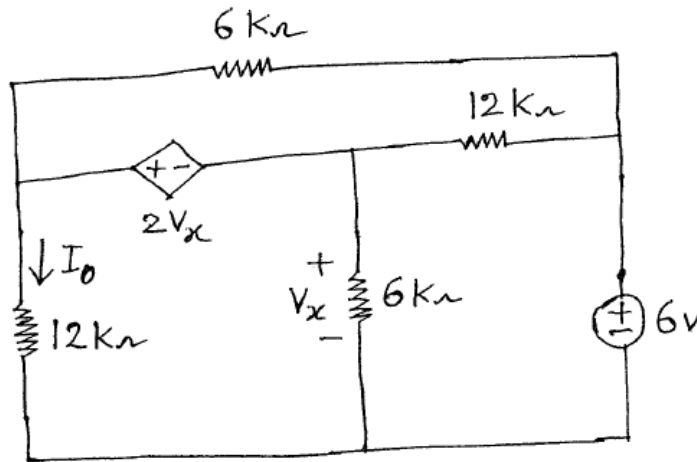
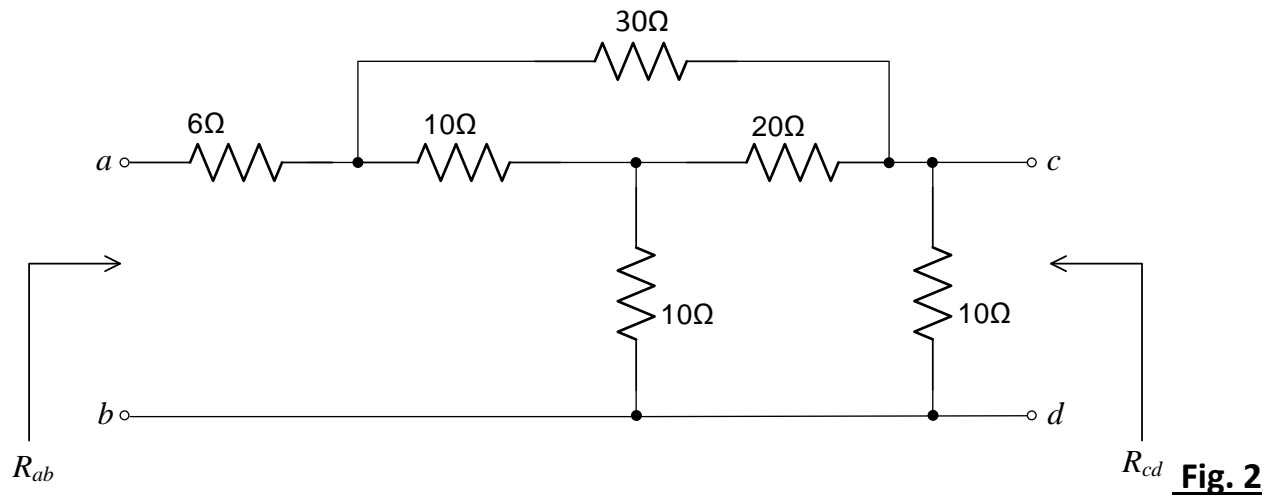



Fig. 1

2. Find out the equivalent resistances R_{ab} and R_{cd} as indicated in the figure shown below using Δ -Y or Y- Δ conversion. [15]

**Fig. 2**

PART B (Total number of questions in this part is **TWO (2)**; answer any **ONE (1)** question)

3. For the network shown in Fig. 1, find the current I using **Superposition Theorem**. [15]

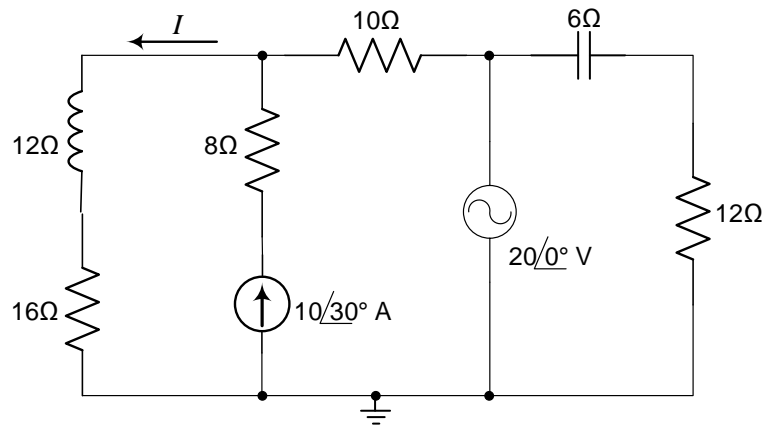**Fig. 3**

4. Consider the following network shown in Fig. 4.

[15]

- Find the Thevenin's equivalent circuit between the terminals a and b.
- Find the load impedance for which maximum power will be transferred to the load.

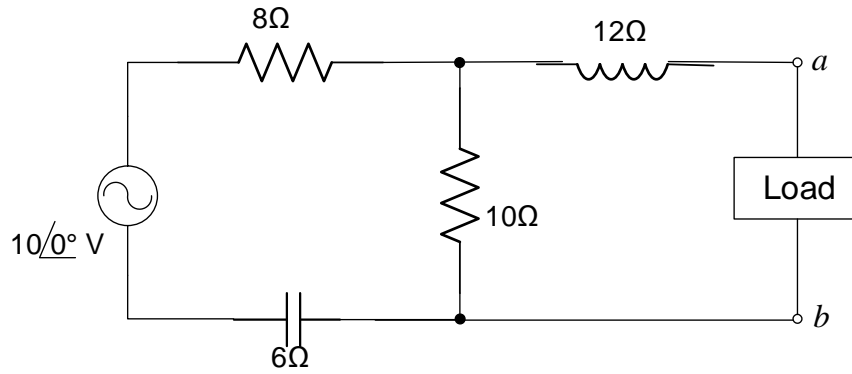


Fig. 4

Section 2

Write an English composition of 200 to 250 words on the topic given below:

**"Being an extrovert is a prerequisite in order to have a successful career."
Do you agree or disagree with the given statement? Explain your views with relevant examples.**